

Contents

- [Assignment 4](#)
- [1. Modelling the Current-Voltage Characteristics & Linear fit to determine the resistance value of the device and use it for R3](#)
- [Defining Circuit Parameters](#)
- [3. Breaking the circuit down into Differential Equations](#)
- [4. Transient Circuit Simulation](#)
- [5. Circuit with Noise](#)
- [5.c.vii. Changing the Time-Step](#)
- [Extra Checks for Section 5](#)
- [6. Non-linearity](#)

Assignment 4

Circuit Modeling

Author: Ragini Bakshi, April 2021

```
set(0,'DefaultFigureWindowState','docked')
set(0,'defaultaxesfontsize',12)
set(0,'defaultaxesfontname','Times New Roman')
set(0,'DefaultLineLineWidth',2);

clear all
close all
```

1. Modelling the Current-Voltage Characteristics & Linear fit to determine the resistance value of the device and use it for R3

using fixed bottleneck and Voltage sweep from 0.1V to 10V

```
steps_for_voltage = 50;
stepped_voltage = linspace(0.1, 10, steps_for_voltage);
for i=1:steps_for_voltage
    [Curr, Vmap, Ex, Ey, eFlowx, eFlowy, Cnx] = current_solver(stepped_voltage(i)); % calls current_solver function from assignment 2
    plotting_current(i) = Cnx;
end

% figure(1)
% plot(plotting_current, stepped_voltage)
r_inv = polyfit(stepped_voltage, plotting_current,1);
r_fitted = 10/r_inv(1); % note: im afraid this is not complete: I ran out of time
%so I've simply obtained the current from the electric field, not the number of particles passing the
%right boundary of the active region and subtracting the ones passing backwards through the left, waiting
%for the simulation to stabilize and then summing the average to get the
%current (involved implementing assignment 3 but its giving an error message so I've left it out).
```

Defining Circuit Parameters

The capacitor and inductor in the circuit give it a Bandpass-like filter. There are no non-linear capacitors

```
R1 = 1;
C_1 = 0.25;
R2 = 2;
L = 0.2;
R3 = r_fitted; % changed this from 10ohms to fitted value using assignment 2
alpha = 100;
R4 = 0.1;
Ro = 1000;

% DC sweep for 100 Vin values
Vin = -10:0.1:10;
%Vin = Vin';
```

3. Breaking the circuit down into Differential Equations

3.a.i. Assuming V_1 is the current that flows thru Node 1, V_2 is the current that flows thru Node 2, I_{in} is the current going into the circuit, I_l is the current thru inductor, etc, the differential equations become:

```

G1 = 1/R1;
G2 = 1/R2;
G3 = 1/R3;
G4 = 1/R4;
Go = 1/Ro;

% V1 = Vin;

% KCL equations for this network:
% G1(V1 - V2) + sC_1(V1 - V2) + Iin = 0;
% G1(V2 - V1) + sC_1(V2 - V1) + V2*G2 + I1 = 0;
% V2 - V3 - sL = 0
% G3*V3 - I1 = 0
% V4 - G3*alpha*V3 = 0
% G4*(V4 - V5) + I_alpha = 0
% G4*(V5 - V4) + V5*Go = 0

% These equations were used to construct the G conductance matrix and the C
% capacitance matrix. The F vector is for the source.
G = zeros(6,6);
C = zeros(6,6);
F = zeros(6,1);

G(1,1) = 1;
G(2,1) = G1;
G(2,2) = -(G1+G2);
G(2,6) = -1;
G(3,3) = -G3;
G(3,6) = 1;
G(4,3) = -G3*alpha;
G(4,4) = 1;
G(5,5) = -(G4+Go);
G(5,4) = G4;
G(6,2) = -1;
G(6,3) = 1;

C(2,1) = C_1;
C(2,2) = -C_1;
C(6,6) = L;

index = 0;
for Vin = linspace(-10,10,100)
    index = index + 1;
    F(1) = Vin;
    V = G\F;
    Vout(index) = V(5);
    V_3(index) = V(3);
    Vin_vector(index) = Vin;
end

% 3.a.ii. Converting to frequency domain requires the taking the time derivative
% which can then be solved for any omega
index = 0;
F(1) = 1;
for w = linspace(0,100,100)
    index = index + 1;
    omega(index) = w;
    V_ac = (G + 1j*omega(index).*C)\F;
    V_out_ac(index) = V_ac(5);
    gain(index) = 20*log10(abs(V_ac(5))/F(1));
end

% 3.a.iii. Writing down the matrices used to describe the network
display('C matrix'); C
display('G matrix'); G
display('F vector'); F

% 3.b.i. Plot 1: Vout vs Vin DC simulation (circuit has some visible gain)
figure
subplot(3,2,1)
plot(Vin_vector, Vout);
title('Vout and V3 vs. Vin DC Sim');
xlabel('Vin (V)');
ylabel('V (V)');
hold on;
plot(Vin_vector, V_3);
legend('Vout', 'V3')
grid on;

```

```

% 3.b.ii. Plot 2: Voltage as a function of omega (going from 0 to 100) with a peak
% at approx 18 showing Bandpass filter-like behaviour
subplot(3,2,2)
plot(omega, abs(V_out_ac));
title('Vout as a function of omega');
xlabel('omega (rad/s)');
ylabel('Vout (V)');
grid on;

% 3.b.ii. Plot 3: Gain in dB
subplot(3,2,3)
plot(omega, gain);
title('Gain Vo/Vin dB');
xlabel('omega (rads/s)');
ylabel('Gain (dB)');
grid on;

% 3.b.iii. Plot 4 and 5: Monte-Carlo simulation of the circuit multiple times with a
% given standard deviation = 0.05 and normal distribution centered around the
% given values of C = 0.25 and Gain figures, with omega = pi
std = 0.05;

index = 0;
for i = linspace(0,100,1000)
    index = index + 1;
    C(2,1) = C_1 + std*randn();
    C(2,2) = -(C_1 + std*randn());
    C(6,6) = L + std*randn();
    C_o(index) = C_1 + std*randn();
    V_vector = (G + 1j*pi.*C_o(index))\F;
    V_vec = (G + 1j*pi.*C)\F;
    gain_d(index) = 20*log10(abs(V_vec(5))/F(1));
end

subplot(3,2,5)
histogram(C_o)
xlim([0.10,0.40])
xlabel('C');
ylabel('Number');
grid on;

subplot(3,2,6)
histogram(gain_d)
xlabel('V_o/V_i (dB)');
ylabel('Number');
grid on;

```

C matrix

C =

0	0	0	0	0	0
0.2500	-0.2500	0	0	0	0
0	0	0	0	0	0
0	0	0	0	0	0
0	0	0	0	0	0
0	0	0	0	0	0.2000

G matrix






G =

1.0000	0	0	0	0	0
1.0000	-1.5000	0	0	0	-1.0000
0	0	-0.0671	0	0	1.0000
0	0	-6.7060	1.0000	0	0
0	0	0	10.0000	-10.0010	0
0	-1.0000	1.0000	0	0	0

F vector

F =

1
0
0
0
0

  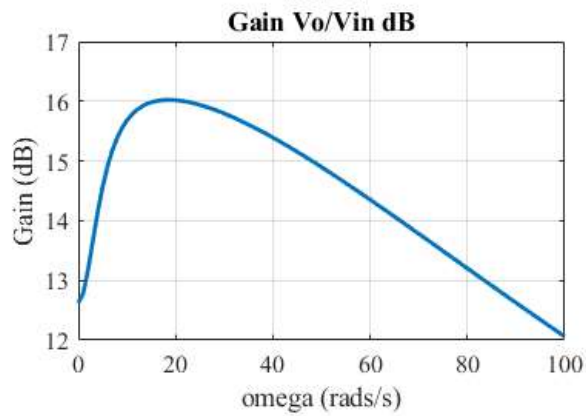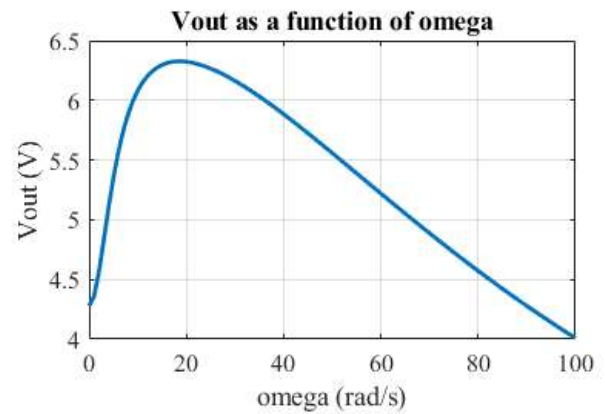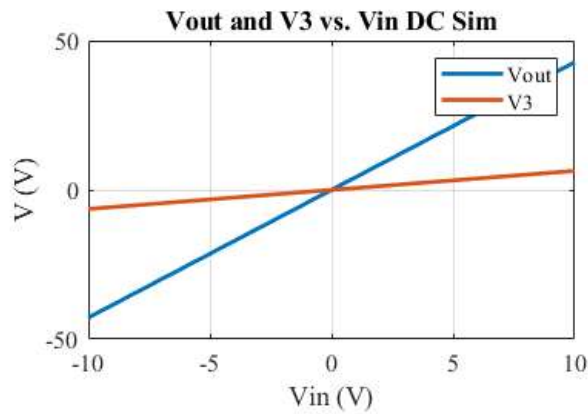

4. Transient Circuit Simulation

```

sim_time = 1;           % simulate for 1s
steps = 1000;           % simulate for 1000 steps
dt = sim_time/steps;    % dt for given time and step size

% Define the 3 types of input signals
Vin_a = zeros(1, steps); % pulse
Vin_b = Vin_a;           % sine
Vin_c = Vin_a;           % gaussian

% Create F, Vout fields
F_a = zeros(6,1);
F_b = zeros(6,1);
F_c = zeros(6,1);

Vout_a = zeros(6, steps);

```

```

Vout_b = zeros(6, steps);
Vout_c = zeros(6, steps);

for i = 1:1:steps-1 % i*dt = time thus col number * dt = current time
    Vout_a(:,1) = 0;
    if ((i+1)*dt) > 0.029
        Vin_a(i+1) = 1;
        F_a(1) = Vin_a(i+1);
        Vout_a(:,i+1) = (C/dt + G) \ (C*Vout_a(:,i)/dt + F_a);
    else % its less than 0.03, should be off
        Vout_a(:,i+1) = (C/dt + G) \ (C*Vout_a(:,i)/dt + F_a);
    end
end

vector = linspace(0,1,steps);

figure(2)
subplot(3,2,1)
hold on;
plot(vector, Vout_a(5,:));
hold on;
grid on;
plot(vector, Vin_a);
hold on;
xlabel('Time (s)');
ylabel('Voltage (V)');
title('Step Function Transient Response');
legend('Vout', 'Vin');

% do fft of pulse here
subplot(3,2,2)
fourier_a_out = 20*log10(abs(fftshift(fft(Vout_a(5,:)))));
fourier_a_in = 20*log10(abs(fftshift(fft(Vin_a))));
fourier_vector = -0.5: dt: 0.5-dt;
plot(fourier_vector, fourier_a_out);
hold on;
grid on;
plot(fourier_vector, fourier_a_in);
xlabel('Freq (Hz)');
ylabel('V (dB)');
legend('Vout', 'Vin');
title('Step Function Frequency Response');

for j = 1:1:steps-1
    Vin_b(j) = sin(2*pi*(j/0.03)*dt);
    if j > 1
        F_b(1,1) = Vin_b(1,j);
        Vout_b(:, j+1) = (C/dt + G) \ (C*Vout_b(:,j)/dt + F_b);
    else % j = 1
        F_b(1,1) = Vin_b(1,1);
        Vout_b(:, j) = (C/dt + G) \ (C*Vout_b(:,1)/dt + F_b);
    end
end

% plot transient of sine here
subplot(3,2,3)
plot(vector, Vout_b(5,:));
hold on;
grid on;
plot(vector, Vin_b)
xlabel('Time (s)');
ylabel('Voltage (V)');
title('Sine Function Transient Response');
legend('Vout', 'Vin');

% do fft of sine here
subplot(3,2,4)
fourier_b_out = 20*log10(abs(fftshift(fft(Vout_b(5,:)))));
fourier_b_in = 20*log10(abs(fftshift(fft(Vin_b))));
plot(fourier_vector, fourier_b_out);
hold on;
grid on;
plot(fourier_vector, fourier_b_in);
xlabel('Freq (Hz)');
ylabel('V (dB)');
legend('Vout', 'Vin');
title('Sine Function Frequency Response');

```

```







Vin_c = gaussmf(vector, [0.03 0.06]);

for k = 1:1:steps-1
    if k > 1
        F_c(1,1) = Vin_c(1,k);
        Vout_c(:, k+1) = (C/dt + G) \ (C*Vout_c(:,k)/dt + F_c);
    else % k = 1
        F_c(1,1) = Vin_c(1,1);
        Vout_c(:, k) = (C/dt + G) \ (C*Vout_c(:,1)/dt + F_c);
    end
end

% plot gaussian here
subplot(3,2,5)
plot(vector, Vout_c(5,:));
hold on;
grid on;
plot(vector, Vin_c)
xlabel('Time (s)');
ylabel('Voltage (V)');
title('Gaussian Input Transient Response');
legend('Vout', 'Vin');

% do fft of gaussian here
subplot(3,2,6)
fourier_c_out = 20*log10(abs(fftshift(fft(Vout_c(5,:)))));
fourier_c_in = 20*log10(abs(fftshift(fft(Vin_c))));
plot(fourier_vector, fourier_c_out);
hold on;
grid on;
plot(fourier_vector, fourier_c_in);
xlabel('Freq (Hz)');
ylabel('V (dB)');
legend('Vout', 'Vin');
title('Gaussian Input Frequency Response');

```

 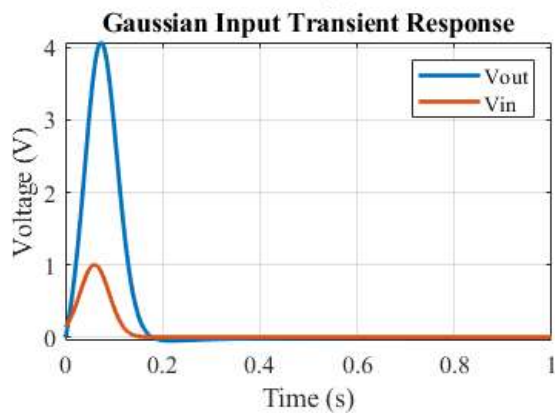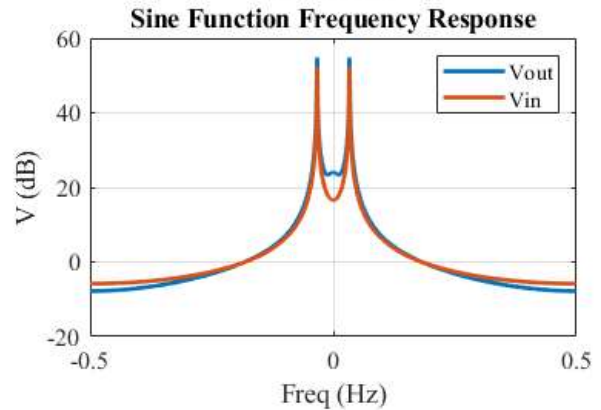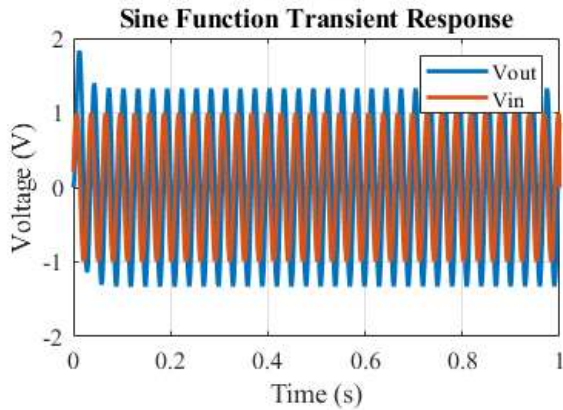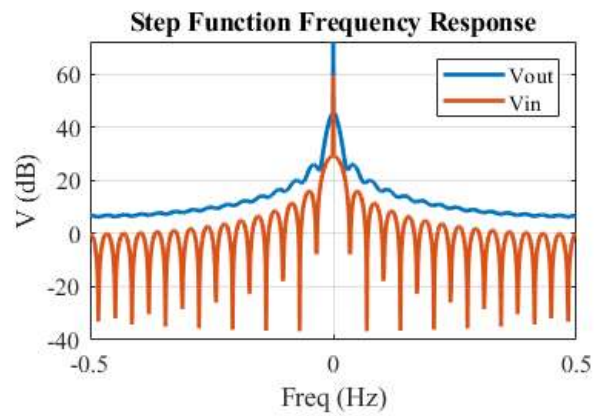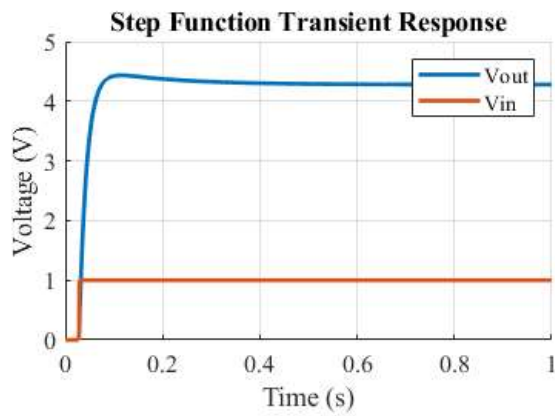

5. Circuit with Noise

A capacitor C_n and current source I_n have been added such that I_n helps model the thermal noise generated in R_3 . This I_n is added in parallel to R_3 in the circuit. C_n acts to limit the noise and impacts the C matrix by adding an extra KCL equation to the circuit representation. C_noise , F_noise and G_noise are defined here again since I did this question separate from part 4 but compiled the 2 scripts for final submission

```
Cn = 0.00001;
I_n_trans = 0.001*randn(steps,1);
I_n = I_n_trans';

C_noise = zeros(8,8);
F_noise = zeros(8,1);
G_noise = zeros(8,8);

C_noise(1,1) = C_1;
C_noise(1,2) = -C_1;
C_noise(2,1) = -C_1;
C_noise(2,2) = C_1;
C_noise(6,6) = -L;
C_noise(3,3) = Cn;
```

```

G_noise(8,1) = 1;
G_noise(8,2) = -1;
G_noise(8,8) = 1;
G_noise(2,1) = -1;
G_noise(2,2) = 1.5;
G_noise(2,6) = 1;
G_noise(3,3) = 0.1;
G_noise(3,6) = -1;
G_noise(4,4) = 10;
G_noise(4,5) = -10;
G_noise(4,7) = 1;
G_noise(5,4) = -10;
G_noise(5,5) = 10;
G_noise(6,2) = 1;
G_noise(6,3) = -1;
G_noise(7,3) = -10;
G_noise(7,4) = 1;
G_noise(1,1) = 1;

% 5.a. Updated C matrix
display('C matrix with noise'); C_noise
%display('G matrix with noise'); G_noise

Vout_noise = zeros(8,steps);

for m = 1:1:steps-1
    if m > 1
        F_noise(1,1) = Vin_c(1,m);
        F_noise(3,1) = -I_n(1,m);
        Vout_noise(:, m+1) = (C_noise/dt + G_noise) \ (C_noise*Vout_noise(:,m)/dt + F_noise);
    else % m = 1
        F_noise(1,1) = Vin_c(1,1);
        Vout_noise(:, m) = (C_noise/dt + G_noise) \ (C_noise*Vout_noise(:,1)/dt + F_noise);
    end
end

% plot of gaussian
figure(3)
subplot(3,2,1)
plot(vector, Vout_noise(5,:));
hold on;
grid on;
plot(vector, Vin_c)
xlabel('Time (s)');
ylabel('Voltage (V)');
title({
    ['Gaussian Input Transient Response with Noise']
    ['C_n = 0.00001']
});
legend('Vout', 'Vin');

% fft of gaussian
subplot(3,2,2)
fourier_noise_out = 20*log10(abs(fftshift(fft(Vout_noise(5,:)))));
fourier_noise_in = 20*log10(abs(fftshift(fft(Vin_c))));
plot(fourier_vector, fourier_noise_out);
hold on;
grid on;
plot(fourier_vector, fourier_noise_in);
xlabel('Freq (Hz)');
ylabel('V (dB)');
legend('Vout','Vin');
title({
    ['Gaussian Input Frequency Response with Noise']
    ['C_n = 0.00001']
});

% 5.c.vi. Changing Cn to 10x less the given value
Cn = 0.000001;
C_noise(3,3) = Cn;

for m = 1:1:steps-1
    if m > 1
        F_noise(1,1) = Vin_c(1,m);
        F_noise(3,1) = -I_n(1,m);
        Vout_noise(:, m+1) = (C_noise/dt + G_noise) \ (C_noise*Vout_noise(:,m)/dt + F_noise);
    else % m = 1
        F_noise(1,1) = Vin_c(1,1);
        Vout_noise(:, m) = (C_noise/dt + G_noise) \ (C_noise*Vout_noise(:,1)/dt + F_noise);
    end
end

```



```

        end
    end

% plot gaussian here
figure(3)
subplot(3,2,3)
plot(vector, Vout_noise(5,:));
hold on;
grid on;
plot(vector, Vin_c)
xlabel('Time (s)');
ylabel('Voltage (V)');
title({
    ['Gaussian Input Transient Response with Noise']
    ['C_n = 10x less']
});
%subtitle('C_n = 10x less');
legend('Vout', 'Vin');

% fft of gaussian here
subplot(3,2,4)
fourier_noise_out = 20*log10(abs(fftshift(fft(Vout_noise(5,:)))));
fourier_noise_in = 20*log10(abs(fftshift(fft(Vin_c))));
plot(fourier_vector, fourier_noise_out);
hold on;
grid on;
plot(fourier_vector, fourier_noise_in);
xlabel('Freq (Hz)');
ylabel('V (dB)');
legend('Vout', 'Vin');
title({
    ['Gaussian Input Frequency Response with Noise']
    ['C_n = 10x less']
});

% 5.c.vi. Changing Cn to 5x greater than the given value
Cn = 0.00005;
C_noise(3,3) = Cn;

for m = 1:1:steps-1
    if m > 1
        F_noise(1,1) = Vin_c(1,m);
        F_noise(3,1) = -I_n(1,m);
        Vout_noise(:, m+1) = (C_noise/dt + G_noise) \ (C_noise*Vout_noise(:,m)/dt + F_noise);
    else % m = 1
        F_noise(1,1) = Vin_c(1,1);
        Vout_noise(:, m) = (C_noise/dt + G_noise) \ (C_noise*Vout_noise(:,1)/dt + F_noise);
    end
end

% plot gaussian here
subplot(3,2,5)
plot(vector, Vout_noise(5,:));
hold on;
grid on;
plot(vector, Vin_c)
xlabel('Time (s)');
ylabel('Voltage (V)');
title({
    ['Gaussian Input Transient Response with Noise']
    ['C_n = 5x more']
});
legend('Vout', 'Vin');

% fft of gaussian here
subplot(3,2,6)
fourier_noise_out = 20*log10(abs(fftshift(fft(Vout_noise(5,:)))));
fourier_noise_in = 20*log10(abs(fftshift(fft(Vin_c))));
plot(fourier_vector, fourier_noise_out);
hold on;
grid on;
plot(fourier_vector, fourier_noise_in);
xlabel('Freq (Hz)');
ylabel('V (dB)');
legend('Vout', 'Vin');
title({
    ['Gaussian Input Frequency Response with Noise']
    ['C_n = 5x more']
});

```

```
% Observations: for a larger Cn value larger noise values are removed from
% the system and thus the bandwidth is a bit smaller compared to normal
% (note figure 3, subplot #5 has the least amount of noise (clear in the
% time domain) compared to the other 2).
% For smaller Cn the opposite effect occurs and the bandwidth is larger.
```

C matrix with noise







C_noise =

Columns 1 through 7

0.2500	-0.2500	0	0	0	0	0
-0.2500	0.2500	0	0	0	0	0
0	0	0.0000	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	-0.2000	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0

Column 8

0
0
0
0
0
0
0
0

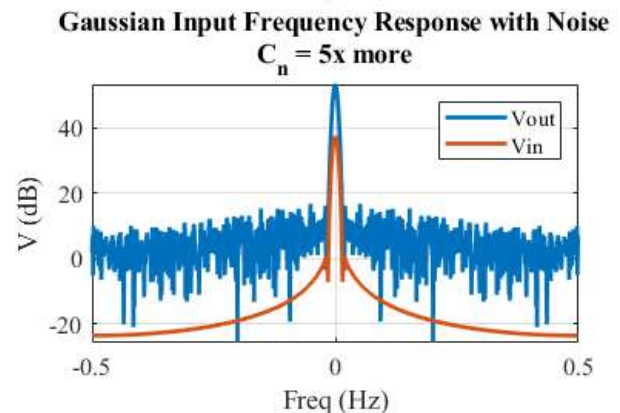 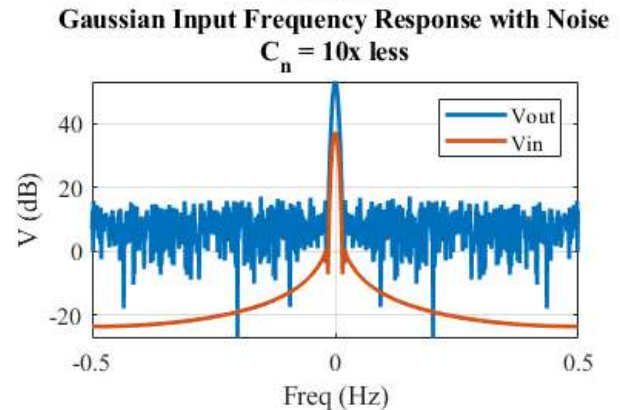  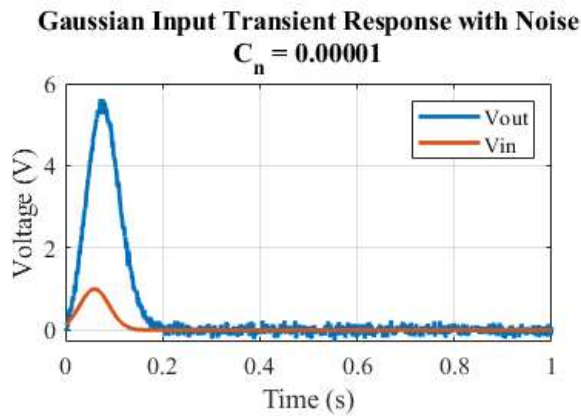

5.c.vii. Changing the Time-Step

Two new time steps were used here: 100 and 5000. These are plotted in addition to 1000 in the time and frequency domain for a gaussian input. I tried to make a function that would do the looping based on step size and that is being called here: `step_solver`. Note that a larger step size = smaller `dt` = better plotting resolution.

```
% Reset Cn and C matrix to Cn = 0.00001
Cn = 0.00001;
C_noise(3,3) = Cn;

% call the step solving function with 5000, 1000, 100 step inputs
[vector_1, Vout_1, I_new_1] = step_solver(C_noise, G_noise, 5000);
[vector_2, Vout_2, I_new_2] = step_solver(C_noise, G_noise, 1000);
[vector_3, Vout_3, I_new_3] = step_solver(C_noise, G_noise, 100);

% 5.c.vii. plot of Vout with varying time steps
figure(4)
plot(vector_1, Vout_1(5,:))
hold on;
plot(vector_2, Vout_2(5,:))
hold on;
plot(vector_3, Vout_3(5,:))
```

```

grid on;
legend('5000 Steps', '1000 Steps', '100 Steps')
xlabel('Time (s)');
ylabel('Voltage (V)');
title('Gaussian Input Transient Response with Noise for varying Time Steps');

% 5.c.vii. frequency plot of Vout for varying time steps
figure(5)
fourier_noise_5k = 20*log10(abs(fftshift(fft(Vout_1(5,:)))));
fourier_noise_1k = 20*log10(abs(fftshift(fft(Vout_2(5,:)))));
fourier_noise_100 = 20*log10(abs(fftshift(fft(Vout_3(5,:)))));
plot(vector_1, fourier_noise_5k);
hold on;
grid on;
plot(vector_2, fourier_noise_1k);
hold on;
plot(vector_3, fourier_noise_100);
xlabel('Freq (Hz)');
ylabel('V (dB)');
legend('5000 Steps', '1000 Steps', '100 Steps');
title('Gaussian Input Frequency Response with Noise for varying Time Steps');

```

Extra Checks for Section 5

Not a part of the assignment, used for debugging purposes only

```

% Uncomment to output check for: are the noise values for different steps
% bandlimited by capacitor
% figure(6)
% plot(vector_1, I_new_1)
% hold on;
% plot(vector_2, I_new_2)
% hold on;
% plot(vector_3, I_new_3)
% grid on;
% legend('5000 Steps', '1000 Steps', '100 Steps');
% title({
%     ['I_n values plotted for each step size confirming that']
%     ['noise is bandlimited by the capacitor in parallel with the noisy resistor']
% });

% Uncomment to output check for: is randn() is returning pseudorandom normally distributed values
% figure(7)
% subplot(1,3,1)
% histogram(I_new_1)
% title('5000 Steps');
% subplot(1,3,2)
% histogram(I_new_2)
% title('1000 Steps');
% subplot(1,3,3)
% histogram(I_new_3)
% title('100 Steps');

```

6. Non-linearity

If the voltage source on the output stage described by the transconductance equation: $V = \alpha I_3$ is changed to the new equation: $V = \alpha I_3 + \beta(I_3)^2 + \gamma(I_3)^3$ then in addition to the G (conductance matrix), C(capacitance matrix), F(time-varying vector with independent sources), we will need to create a "B" non-linear vector to hold the new equation. Since the circuit is now non-linear, frequency analysis will have to be performed to get the soln for an operating point (ex. t=0) and a Jacobean can then find the non-linear solution. An iterative solution at each time step would need to be implemented using Newton-Raphson method. For it to properly converge, we can add an additional G_min conductance. The new MNA matrix equation to be solved is of the form: $CdV/dt + GV + B = F$ and to get the new Voltage, the B vector must be included in the main loops used in this assignment that solve for V. For example, in line 196, new $V_{out_a}(i,i+1) = (C/dt + G) \setminus (C*V_{out_a}(i,i)/dt + F_a - B)$;

From Assignment 2

```

function [Curr, Vmap, Ex, Ey, eFlowx, eFlowy, Cnx] = current_solver(steppped_voltage)
%current_solver
% Inputs: stepped_voltage = the present voltage value that goes from 0.1 to
% 10V (assignment 4 specs)
% Outputs: Cnx = average Current for that Voltage value
%         Curr, Vmap, Ex, Ey, eFlowx, eFlowy

Len = 200e-9;
Wid = 100e-9;
ny = 200;
nx = 100;

```

```

G = sparse(ny*nx, ny*nx);
V = zeros(nx*ny,1);
boundary_condition = [1 1 0 0];
part = 3;

cMap = zeros(nx, ny);
boxL = round(0.4*nx);
boxR = round(0.6*nx);
boxT = round(0.6*ny);
boxB = round(0.4*ny);

for i = 1:nx
    for j = 1:ny
        cMap(i,j) = 1; % outside the box
        if ((i>=boxL && i<=boxR && j>=boxT) || (i>=boxL && i<=boxR && j<=boxB ))
            cMap(i,j) = 0.01; % inside the box
        end
    end
end

% figure(1)
% plot(cMap)
%
% figure(2)
% surf(cMap)

% Using Info from Finite Diff LaPlace Lectures Slides 37,39
% G Matrix
for i = 1:nx
    for j = 1:ny
        n = j + (i - 1) * ny;

        if i == 1
            G(n, :) = 0;
            G(n, n) = 1;
            V(n) = stepped_voltage;
        elseif i == nx
            G(n, :) = 0;
            G(n, n) = 1;
        elseif j == 1
            nxm = j + (i - 2) * ny;
            nxp = j + (i) * ny;
            nyp = j + 1 + (i - 1) * ny;

            rxm = (cMap(i, j) + cMap(i - 1, j)) / 2.0;
            rxp = (cMap(i, j) + cMap(i + 1, j)) / 2.0;
            ryp = (cMap(i, j) + cMap(i, j + 1)) / 2.0;

            G(n, n) = -(rxm+rxp+ryp);
            G(n, nxm) = rxm;
            G(n, nxp) = rxp;
            G(n, nyp) = ryp;
        elseif j == ny
            nxm = j + (i - 2) * ny;
            nxp = j + (i) * ny;
            nym = j - 1 + (i - 1) * ny;

            rxm = (cMap(i, j) + cMap(i - 1, j)) / 2.0;
            rxp = (cMap(i, j) + cMap(i + 1, j)) / 2.0;
            rym = (cMap(i, j) + cMap(i, j - 1)) / 2.0;

            G(n, n) = -(rxm + rxp + rym);
            G(n, nxm) = rxm;
            G(n, nxp) = rxp;
            G(n, nym) = rym;
        else
            nxm = j + (i-2)*ny;
            nxp = j + (i)*ny;
            nym = j-1 + (i-1)*ny;
            nyp = j+1 + (i-1)*ny;

            rxm = (cMap(i,j) + cMap(i-1,j))/2.0;
            rxp = (cMap(i,j) + cMap(i+1,j))/2.0;
            rym = (cMap(i,j) + cMap(i,j-1))/2.0;
            ryp = (cMap(i,j) + cMap(i,j+1))/2.0;

            G(n,n) = -(rxm+rxp+rym+ryp);
        end
    end
end

```

```

        G(n,nxm) = rxm;
        G(n,nxp) = rxp;
        G(n,nym) = rym;
        G(n,nyp) = ryp;
    end

end

end

Voltage = G\V;
Vmap = zeros(nx,ny);

% zz = reshape(Voltage,[10,20]); % doesnt work: try loop to reshape vmap
for x = 1:nx
    for y = 1:ny
        n = y + (x-1)*ny;
        Vmap(x,y) = Voltage(n);
    end
end

% figure(3)
% surf(Vmap)

% Perform gradient for Ex and Ey
[Ey, Ex] = gradient(Vmap);

Ex = -Ex;
Ey = -Ey;

% figure(4)
% quiver(Ex', Ey');
% axis([0 nx 0 ny]);

% normalize to get current from current density
eFlowx = cMap.*Ex;
eFlowy = cMap.*Ey;

Curr = [eFlowx(:),eFlowy(:)];

% uncomment here to check that total current, avg of end currents is the same
% C0 = sum(eFlowx(1,:));
% Cnx = sum(eFlowx(nx,:));
% Currentt = (C0 + Cnx) * 0.5;

end

```

```

function [x_axis, output_V, I_new] = step_solver(C_noise, G_noise, step_count)
%Step_Solver takes the C, G, #iterations as input
%   Outputs a vector to be plotted for x-axis, the output voltage, and
%   current noise levels

dt = 1/step_count;                % change dt based on current step size
x_axis = linspace(0,1,step_count); % x values to be plotted from 0s to 1s
input_V = gaussmf(x_axis, [0.03 0.06]); % input function = gaussian for these x-values
output_V = zeros(8,step_count);    % create output vector
F_value = zeros(8,1);              % F vector

I_new = 0.001*randn(1, step_count); % define thermal noise

for k = 1:1:step_count-1
    if k > 1
        F_value(1,1) = input_V(1,k);
        F_value(3,1) = I_new(1,k);
        output_V(:, k+1) = (C_noise/dt + G_noise) \ (C_noise*output_V(:,k)/dt + F_value);
    else % k = 1
        F_value(1,1) = input_V(1,1);
        output_V(:, k) = (C_noise/dt + G_noise) \ (C_noise*output_V(:,1)/dt + F_value);
    end
end
end

```